
Table of Contents

Part 1 & 2: Pa9 and Transient Circuit Simulation	1
Part 3: Circuit with Noise	11
Part 4 Non Linearity	17

Part 1 & 2: Pa9 and Transient Circuit Simulation

The goal of this assignment is to use nodal analysis techniques to analyse circuits. In Part 1 we are given a circuit to simulate that contains resistors, inductors, capacitors, voltage sources and current sources. To effectively model these components the KCL equations were written for the 5 voltage nodes and an 8x8 matrix for the real and imaginary values of the components was created. (G & C matrices)

The first set of testing conditions were a DC voltage sweep from -10V to 10V while recording the circuit gain. An AC frequency sweep of 0 to 50Hz, with random perturbations on the Capacitance while recording the circuit gain.

The next set of testing conditions was to perform transient analysis on the circuit which involved applying three distinct input signals to the circuit and monitoring the frequency and time domain response of the circuit. The three signals were:

1. A step that transistions from 0 to 1 at 0.03s.
2. A $\sin(2\pi f t)$ function with $f = 1/(0.03)$ 1/s
3. A gaussian pulse with a magnitude of 1, std dev. of 0.03s and a delay of 0.06s

The results displayed in this section are: C and G matrices, Plot of DC sweep, Plots from AC case of gain (V_{out}/V_{in}), Plot of V_{in} and V_{out} from numerical solution in time domain, Fourier Transform plots of Frequency response

```
close all
clear all
Part1F()
Part2T()
```

C =

Columns 1 through 7

0.2500	-0.2500	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	-0.2000
0	0	0	0	0	0	0

Column 8

0
0

0
0
0
0
0
0
0



$G =$



Columns 1 through 7



1.0000	-1.0000	0	0	0	1.0000	0
-1.0000	1.5000	0	0	0	0	1.0000
0	0	0.1000	0	0	0	-1.0000
0	0	0	10.0000	-10.0000	0	0
0	0	0	10.0000	10.0010	0	0
1.0000	0	0	0	0	0	0
0	1.0000	-1.0000	0	0	0	0
0	0	-10.0000	1.0000	0	0	0



Column 8



0
0
0
1.0000
0
0
0
0
0

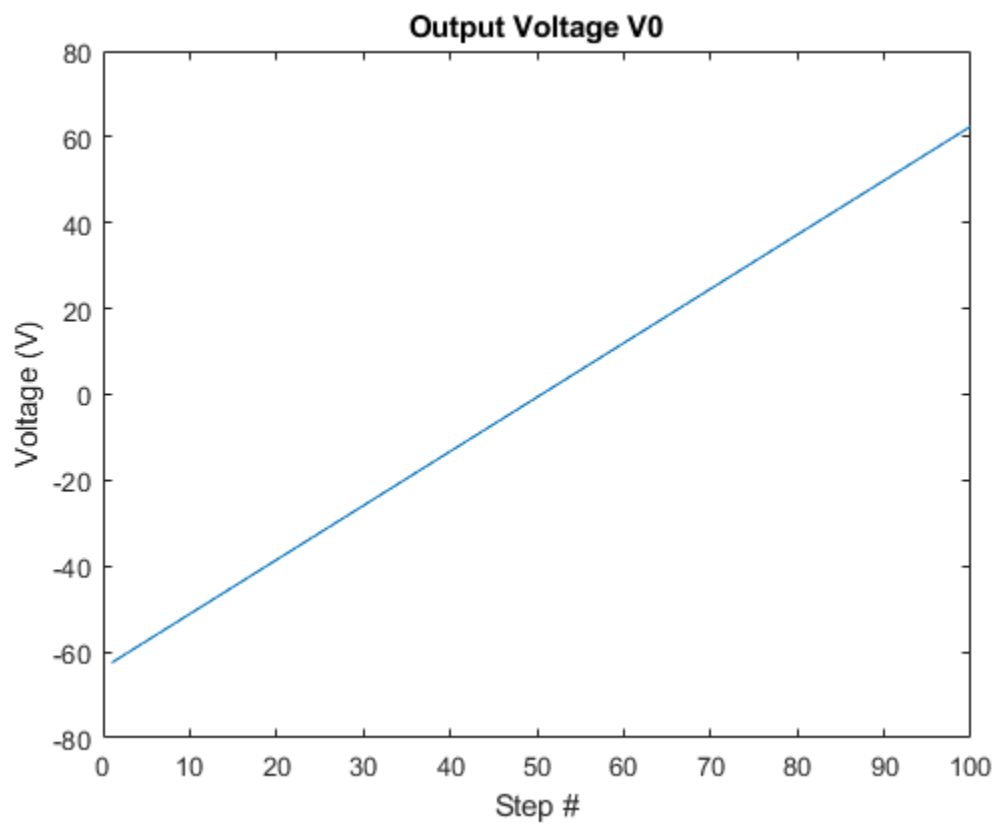
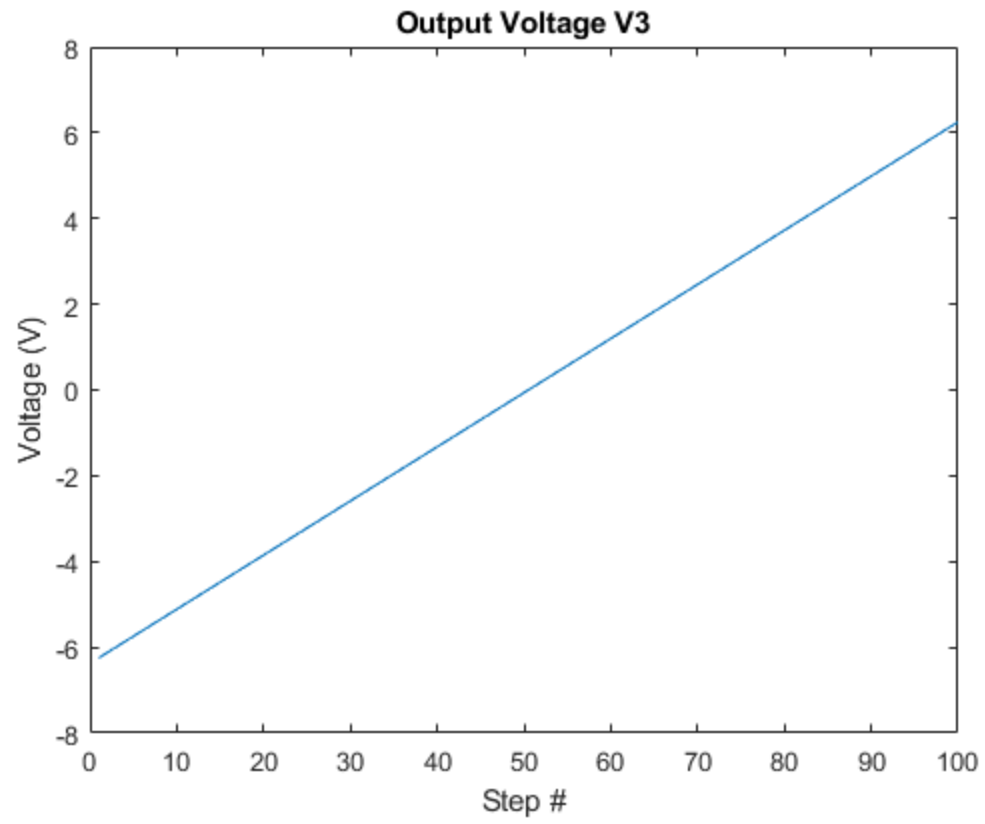


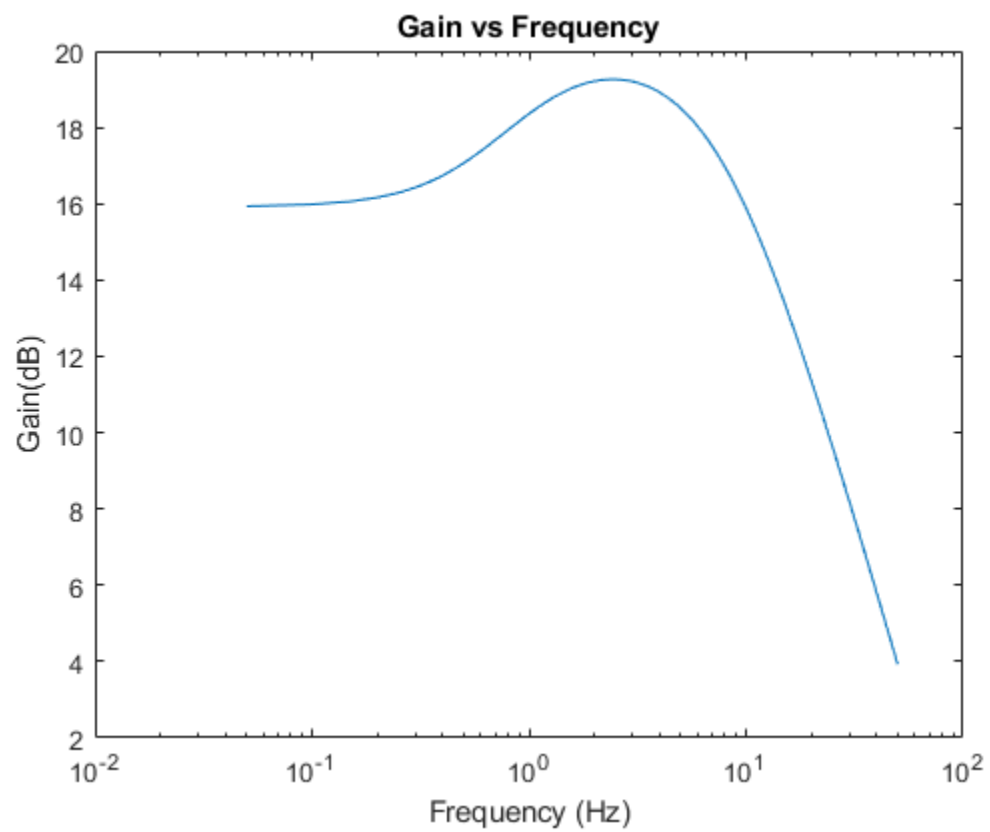
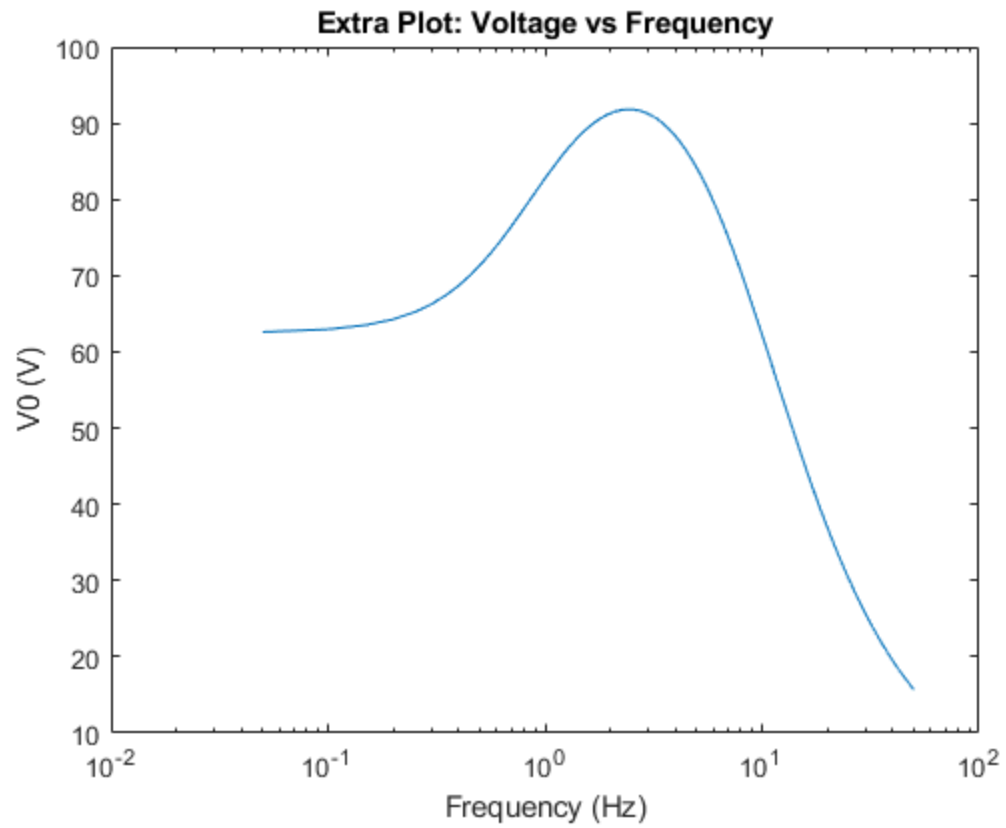


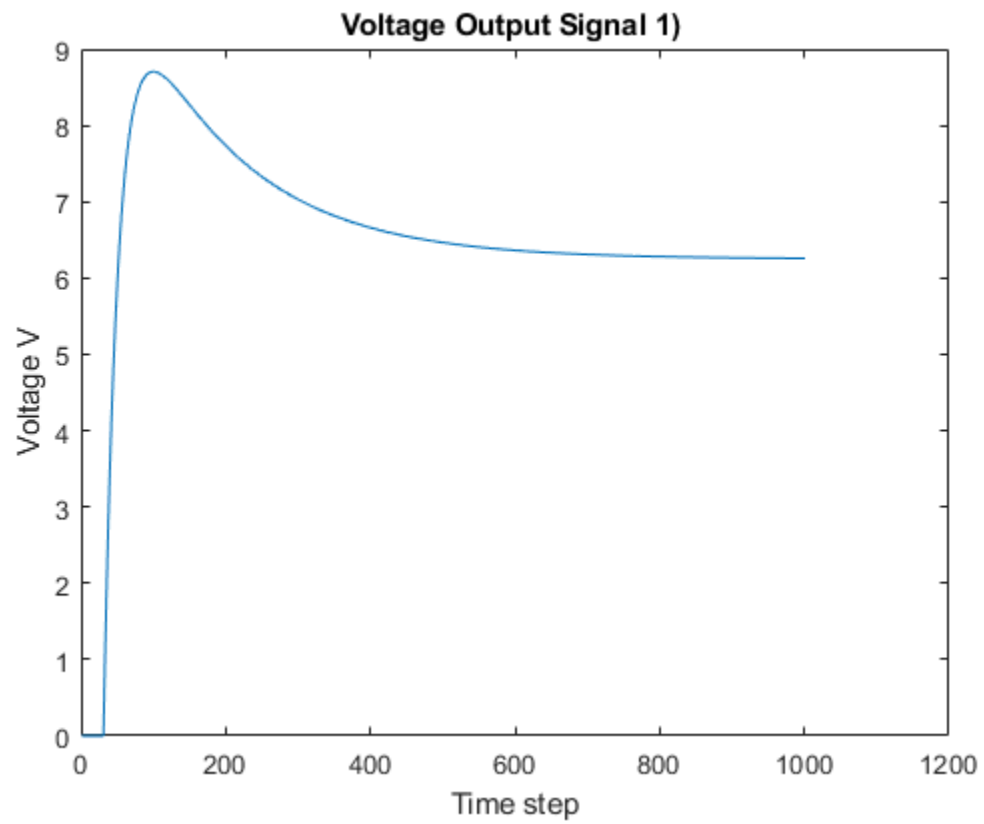
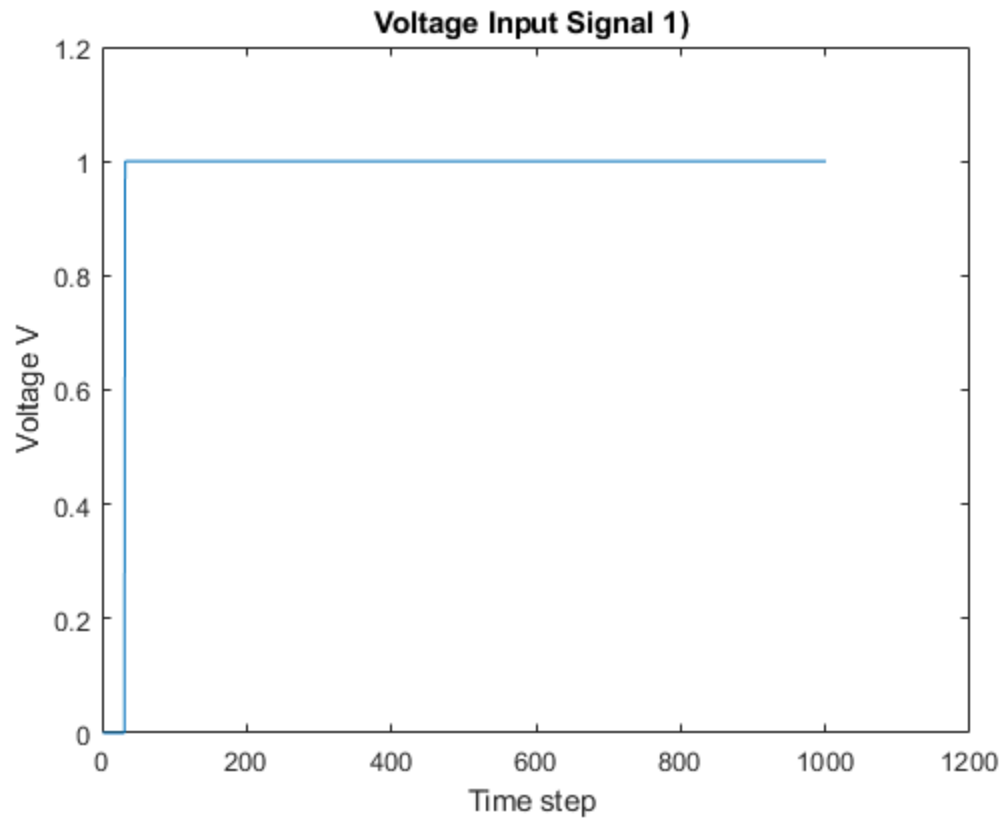


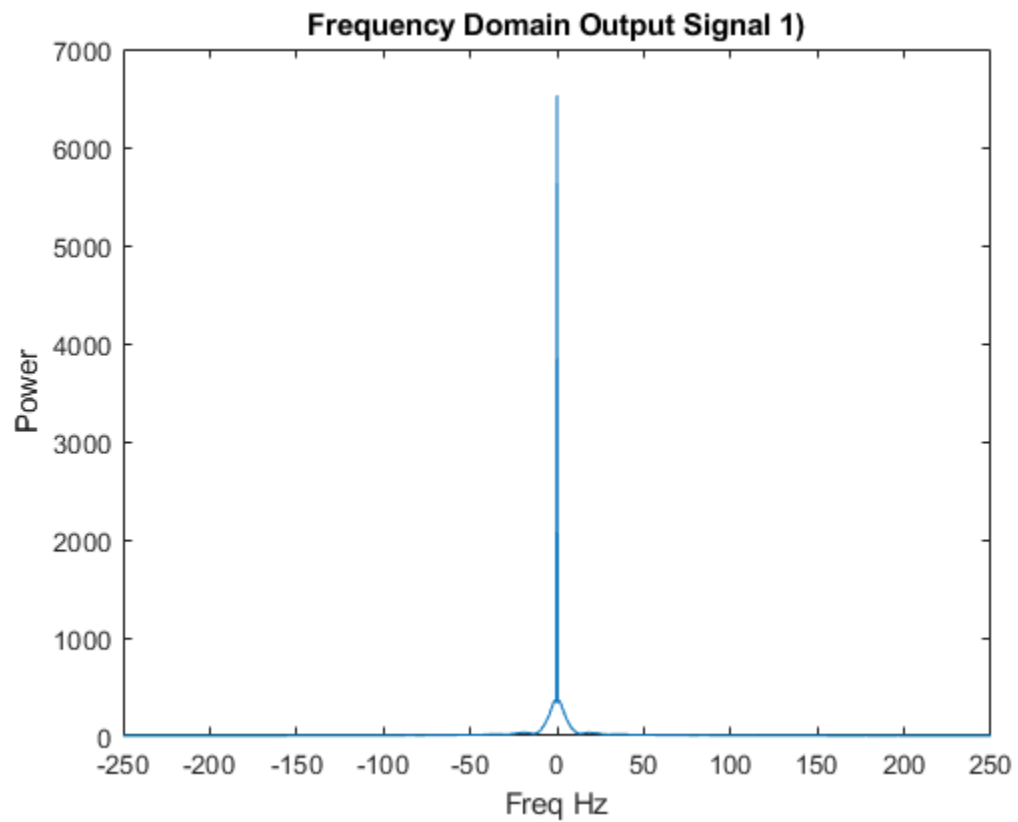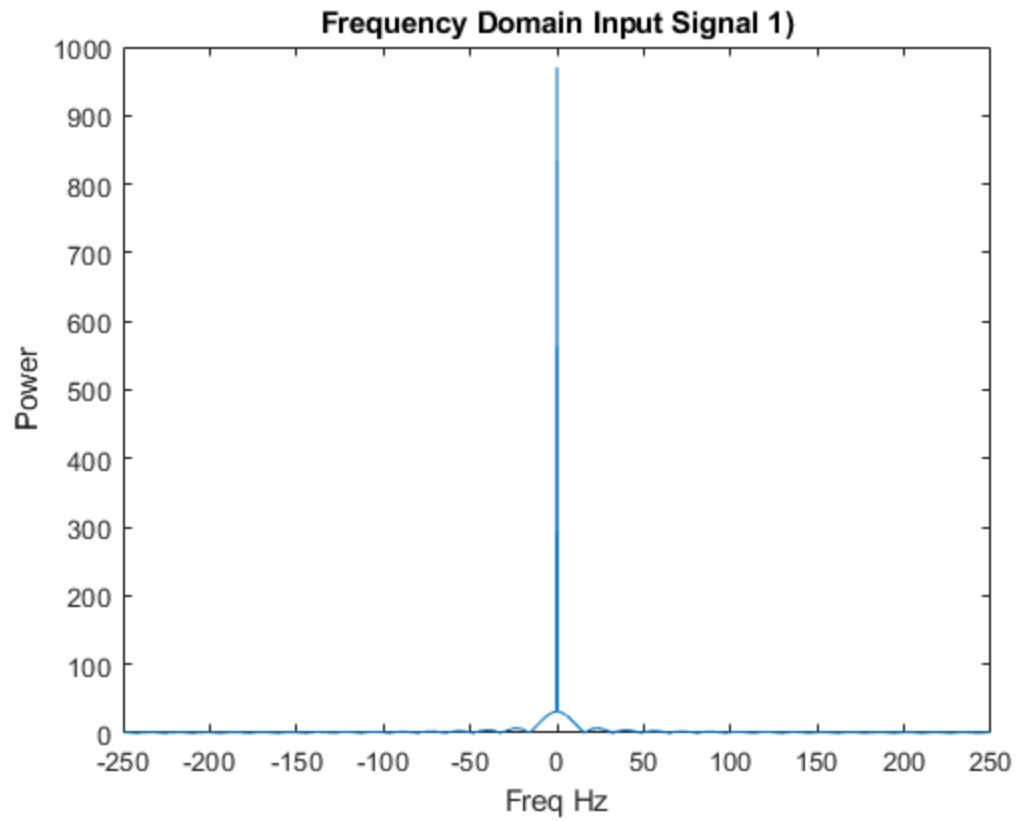

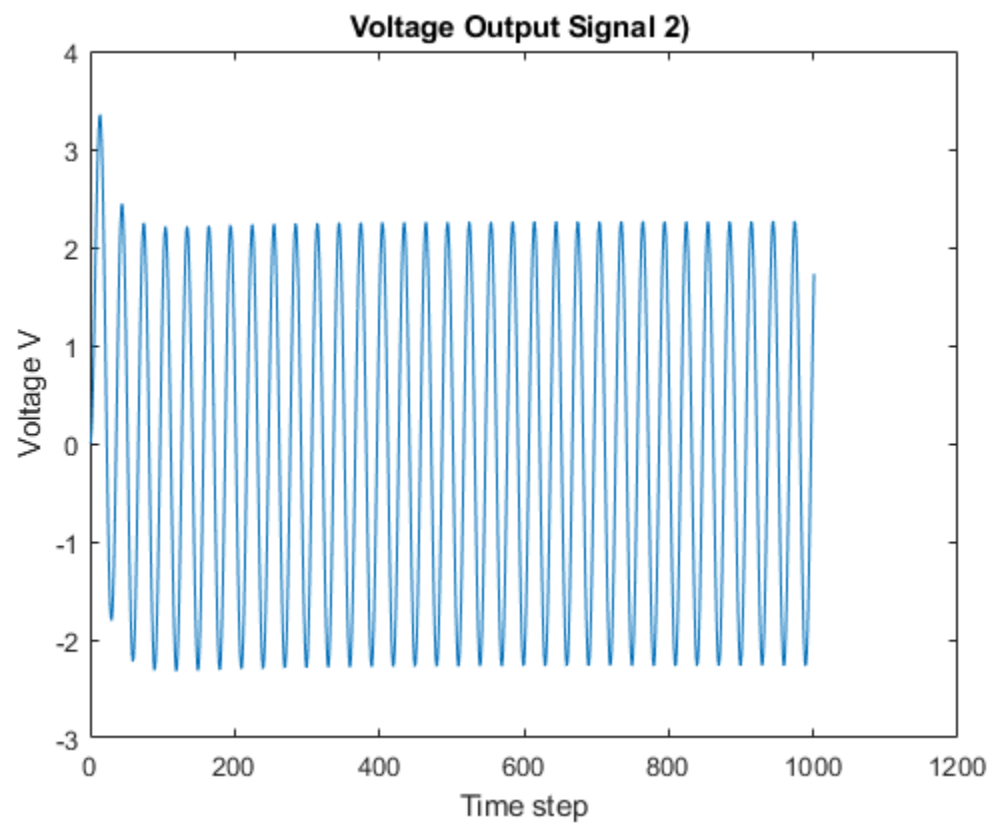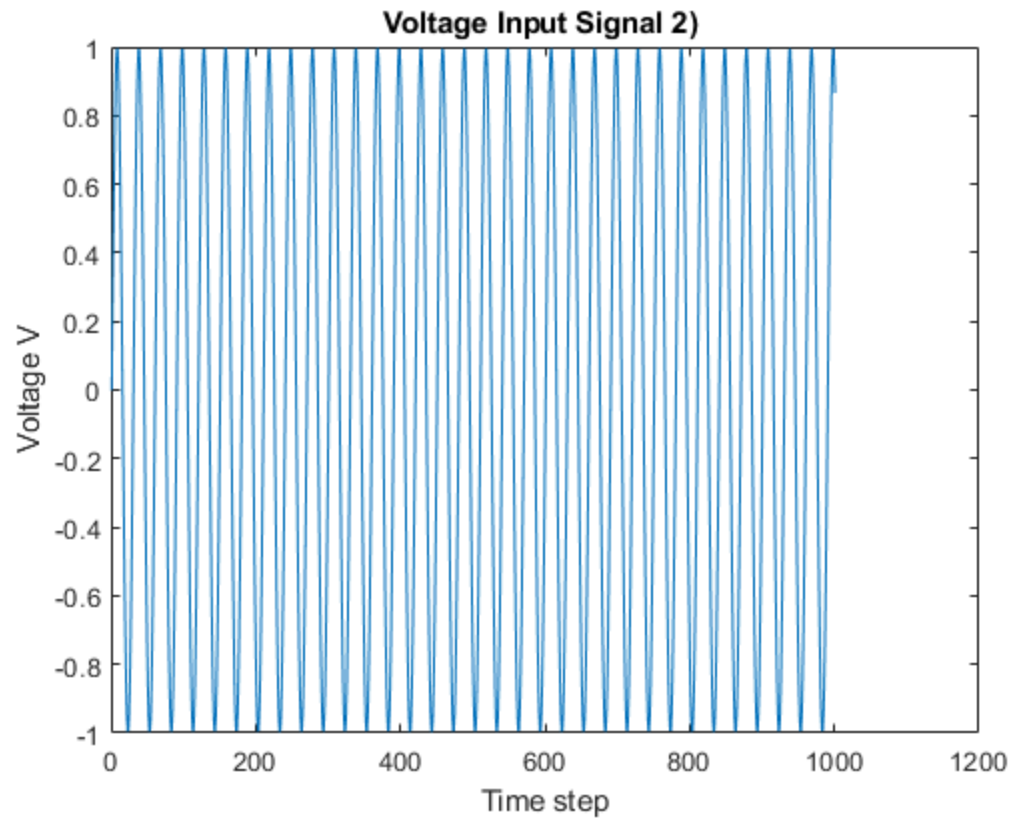

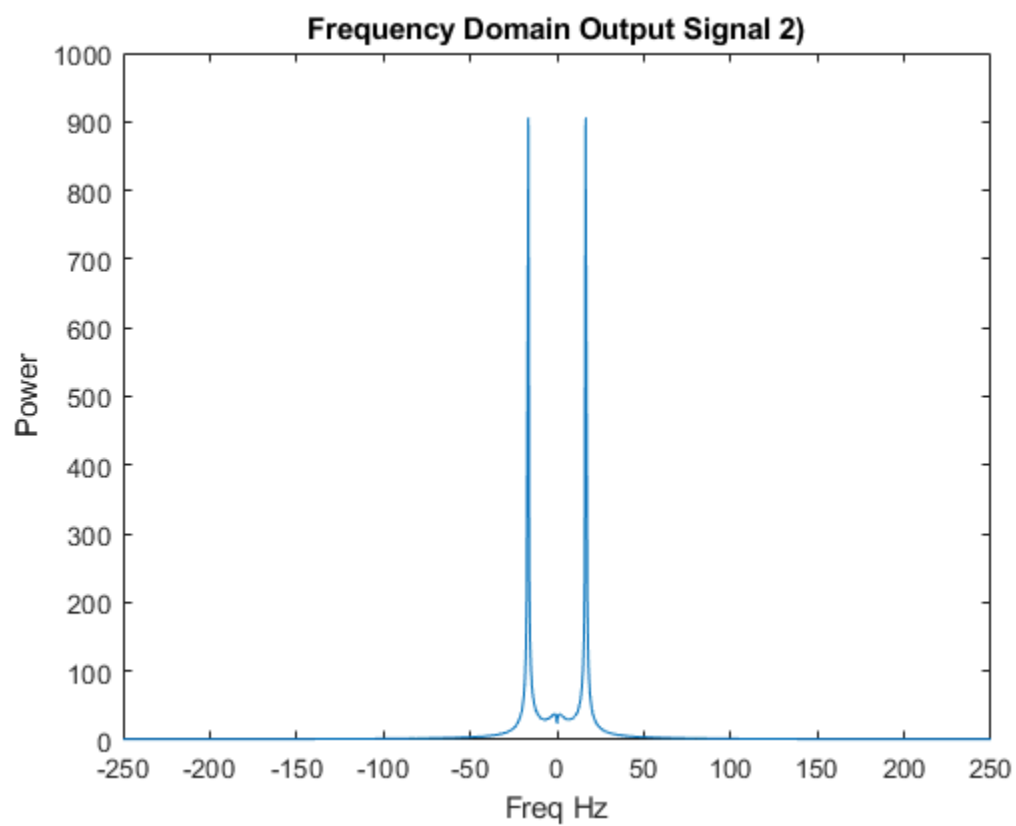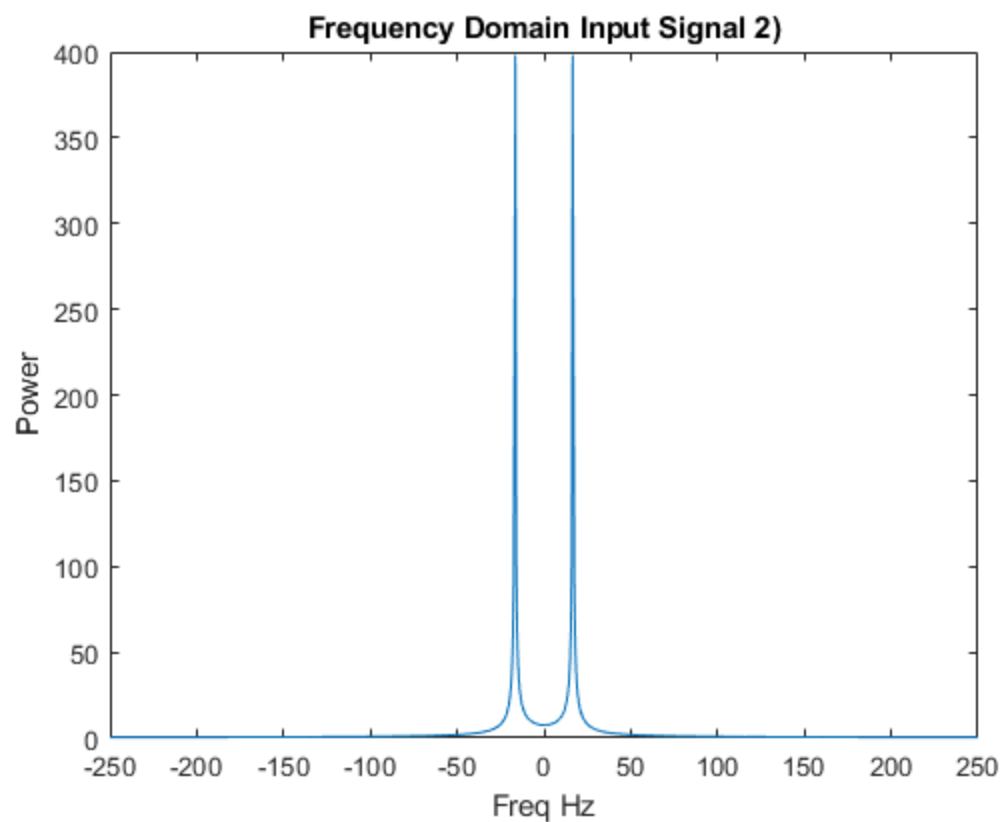

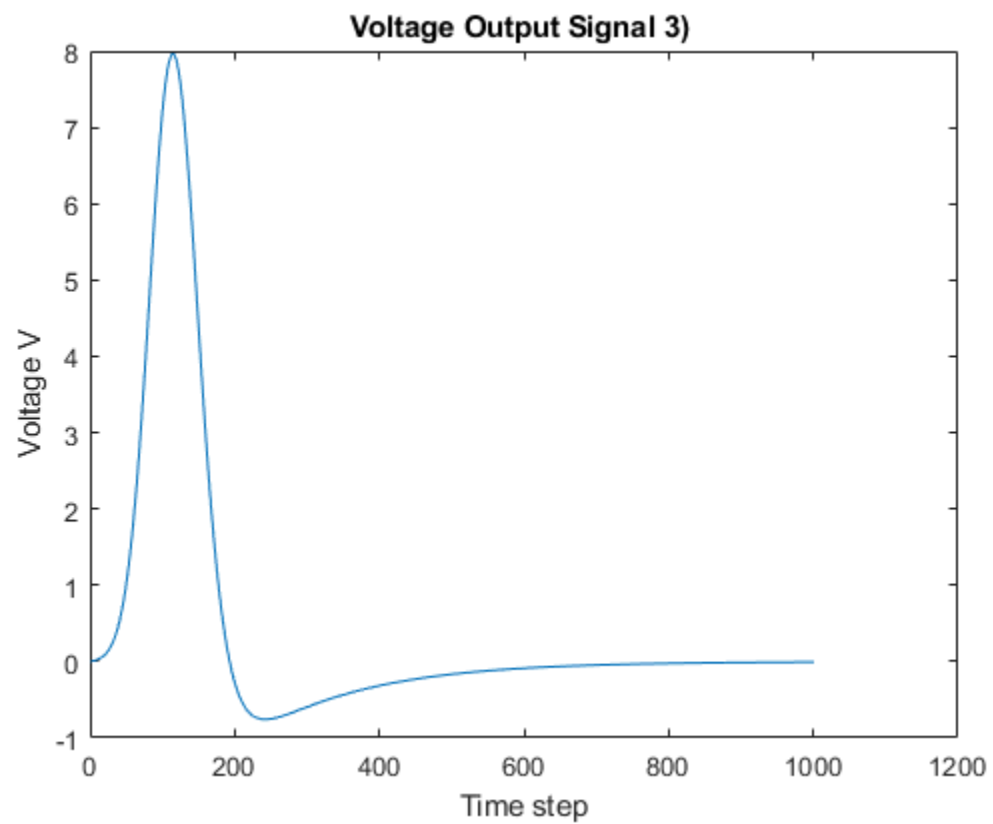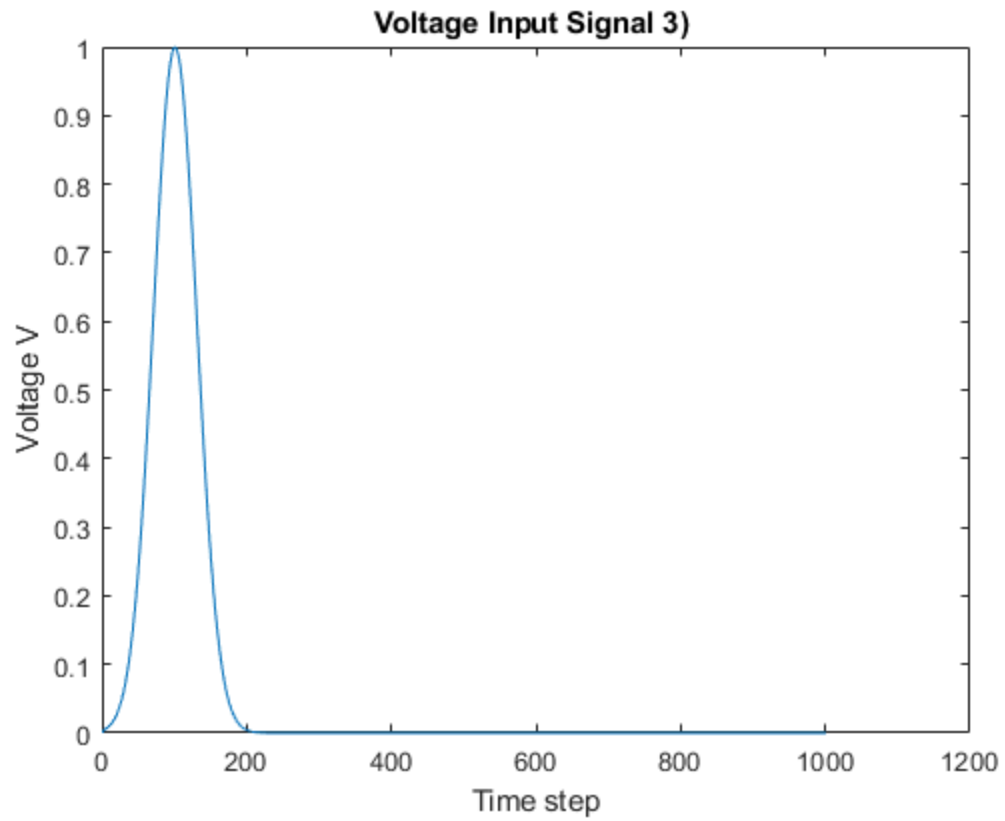

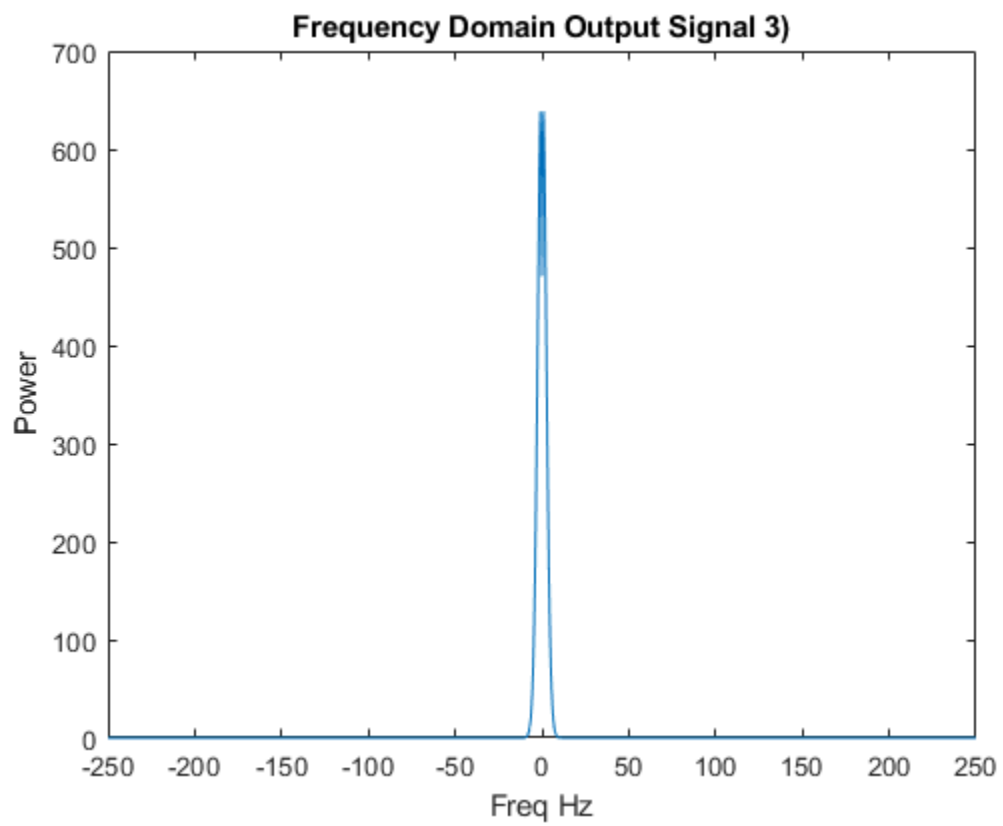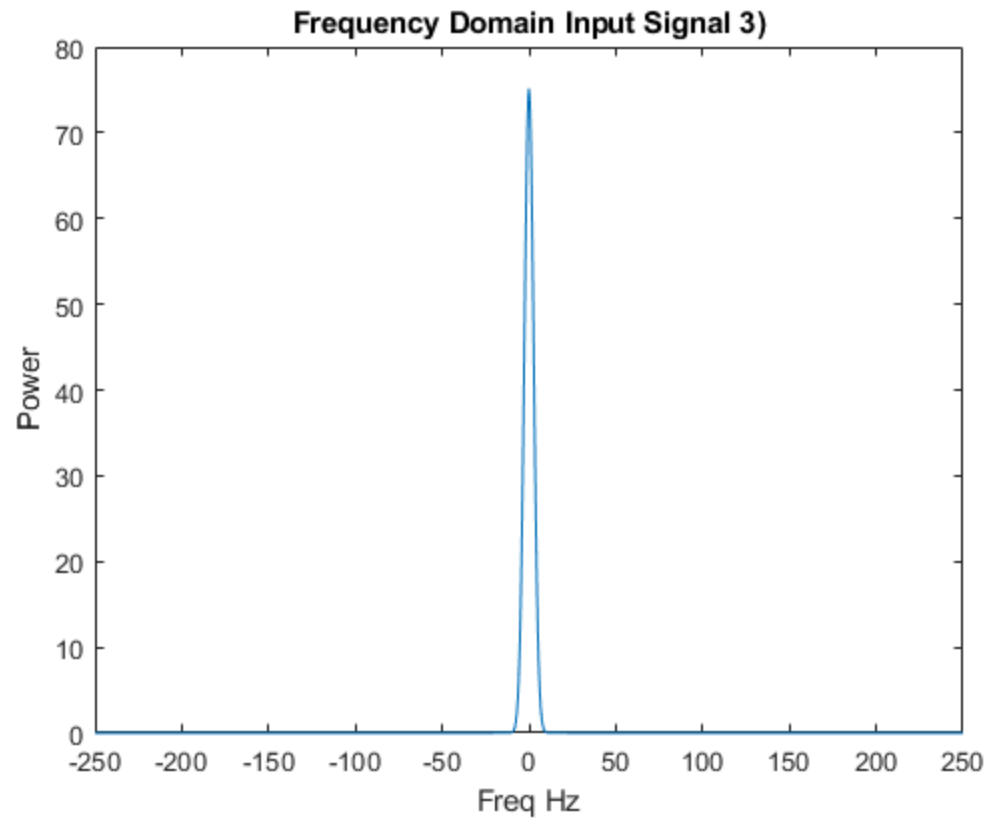

The circuit is linear and this is demonstrated by the DC sweep. We see that the V_{out} is a linear function of the input voltage V_{in} .

Inspecting the frequency sweep, the circuit's gain begins to sharply decrease around 10Hz. What this means is that the circuit is operating like a low pass filter. Lower frequencies are allowed to pass but higher frequencies are attenuated.

When we introduced the random perturbations on the capacitance the gain of the circuit is relatively consistent. This is a benefit because if the circuit were to be manufactured there would surely be unexpected parasitic capacitances and manufacturing variations. The fact that the circuit is not overly sensitive is a valuable characteristic of the circuit.

Part 3: Circuit with Noise

In this section of the assignment we try to model random thermal noise on a resistor by inserting a current source to inject the noise and a capacitor to limit the bandwidth of the noise. The capacitor value used was as given $C_n=0.00001$ and the noise distribution was gaussian with a maximum value of 0.001.

The student performed analysis by recording the output of the circuit in the time and frequency domain (fft). Then the student varied the value of C_n to observe how the bandwidth of the noise affects the circuits operation. Finally the student varied granularity of the time steps to observe how to it affected circuit operation.

```
Part3a()  
Part3b()
```

$G =$

Columns 1 through 7

1.0000	-1.0000	0	0	0	1.0000	0
-1.0000	1.5000	0	0	0	0	1.0000
0	0	0.1000	0	0	0	-1.0000
0	0	0	10.0000	-10.0000	0	0
0	0	0	10.0000	10.0010	0	0
1.0000	0	0	0	0	0	0
0	1.0000	-1.0000	0	0	0	0
0	0	-10.0000	1.0000	0	0	0

Column 8

0
0
0
1.0000
0
0
0
0


$C =$



Columns 1 through 7



0.2500	-0.2500	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0
0	0	0.0000	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	-0.2000
0	0	0	0	0	0	0



Column 8



0
0
0
0
0
0
0
0
0
0

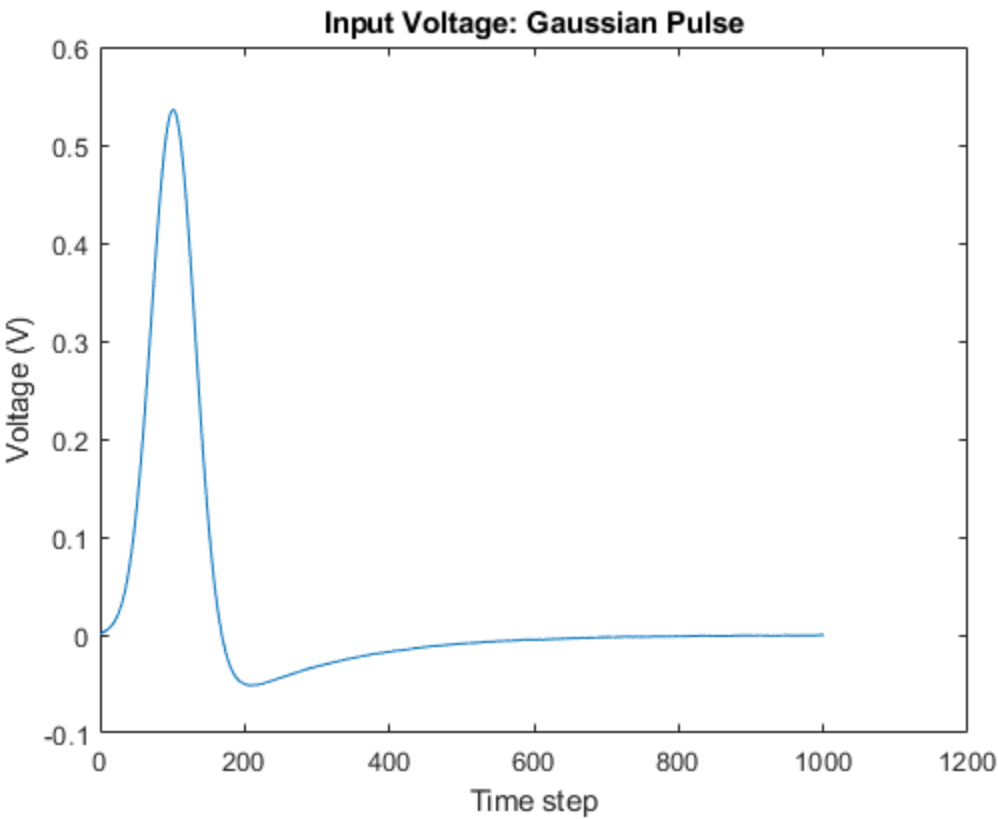


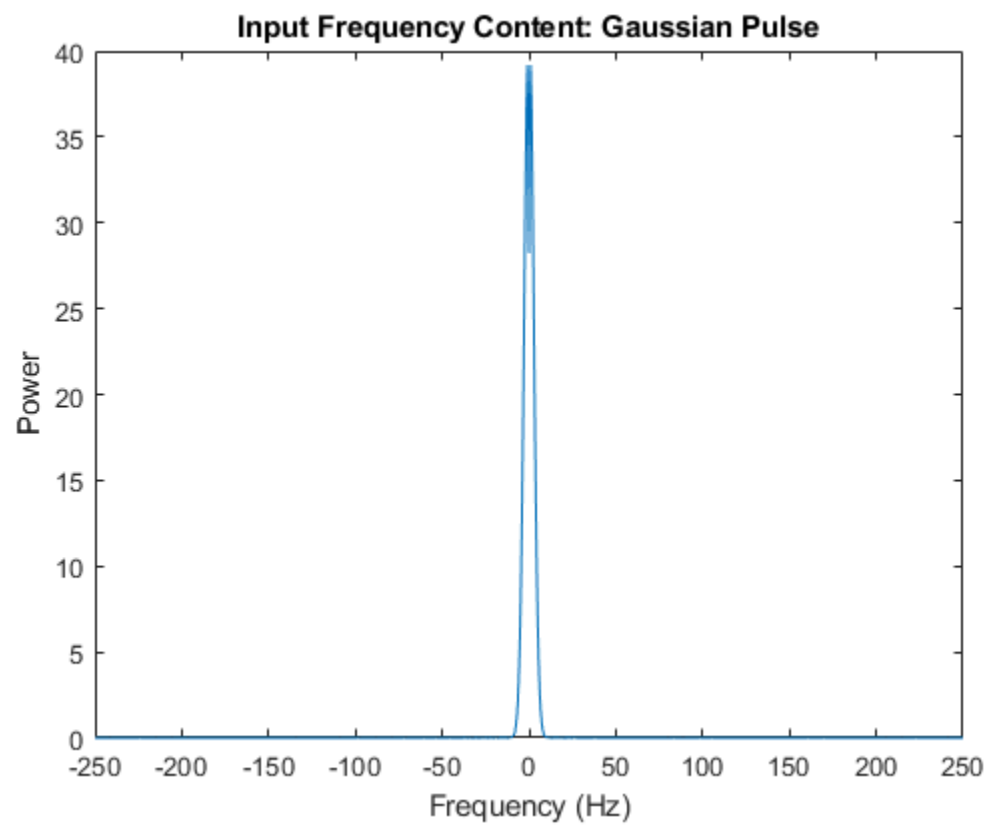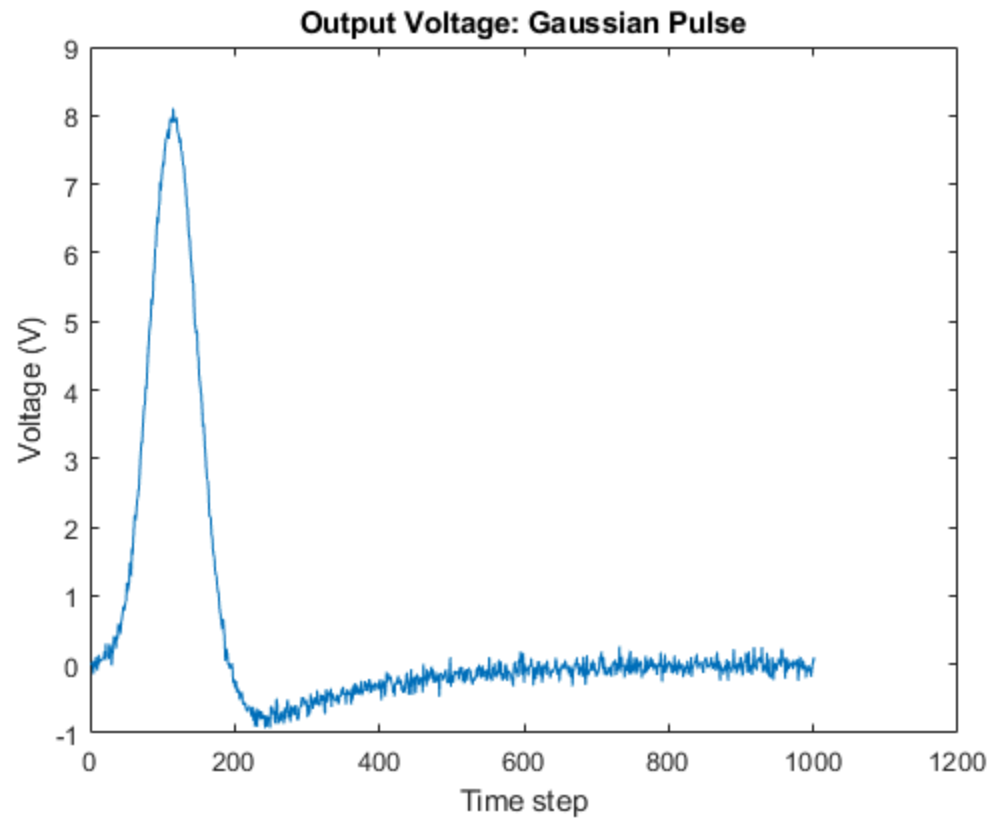

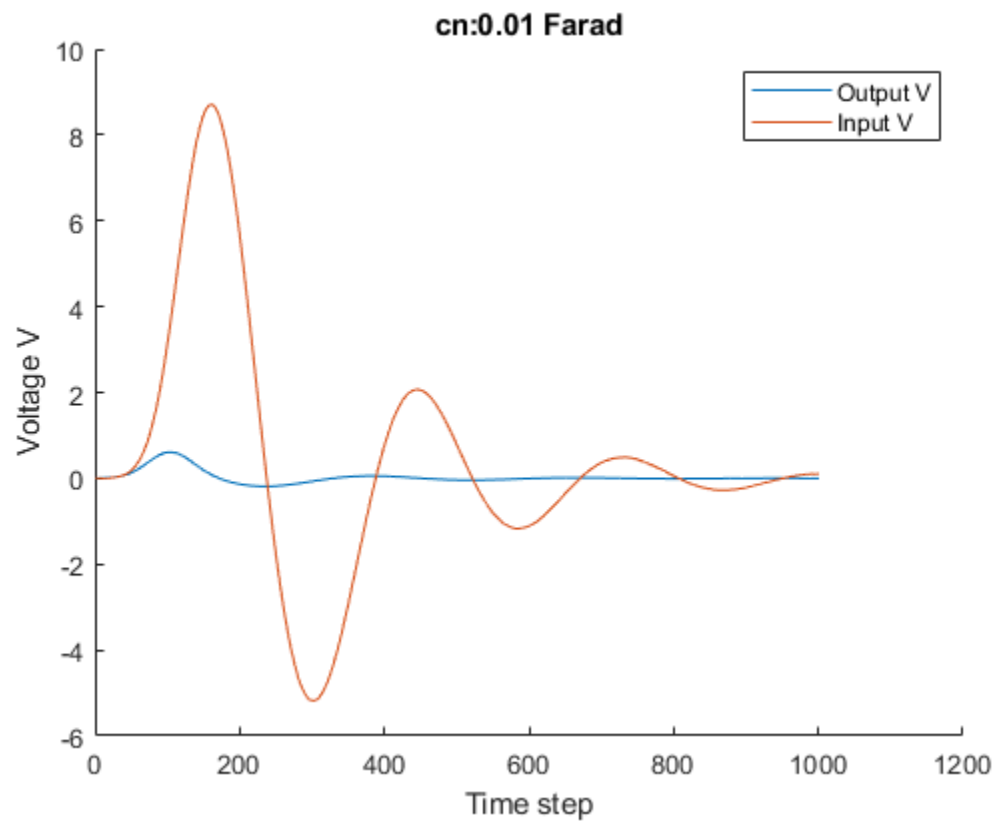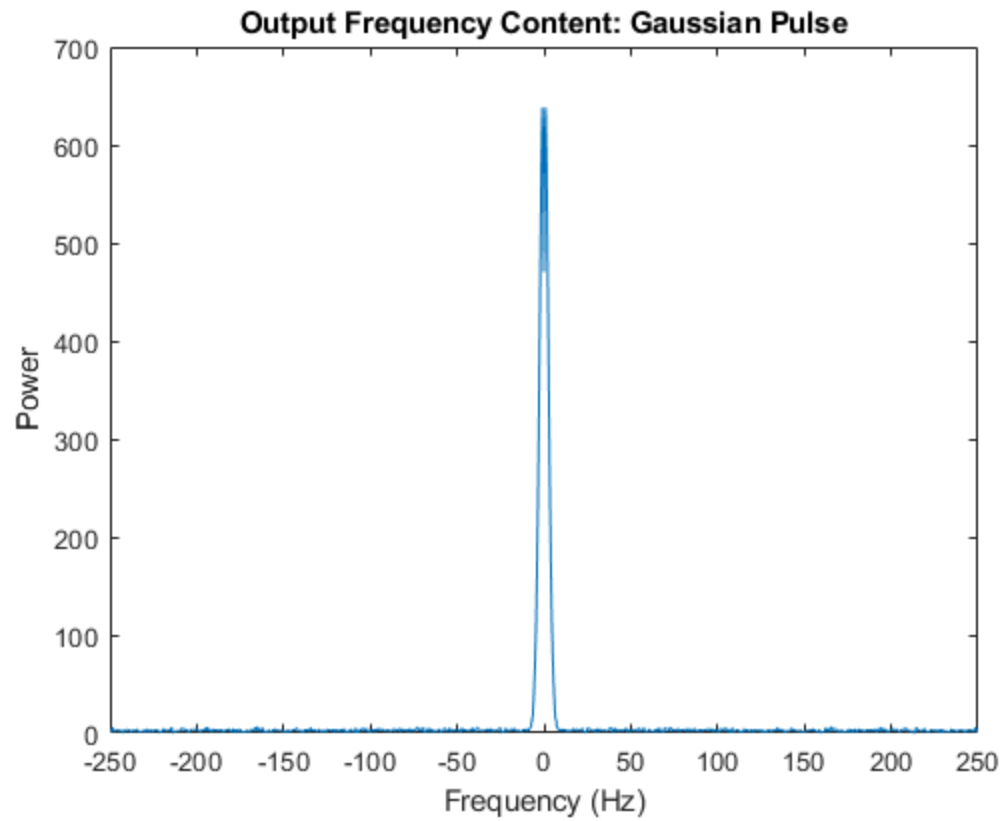

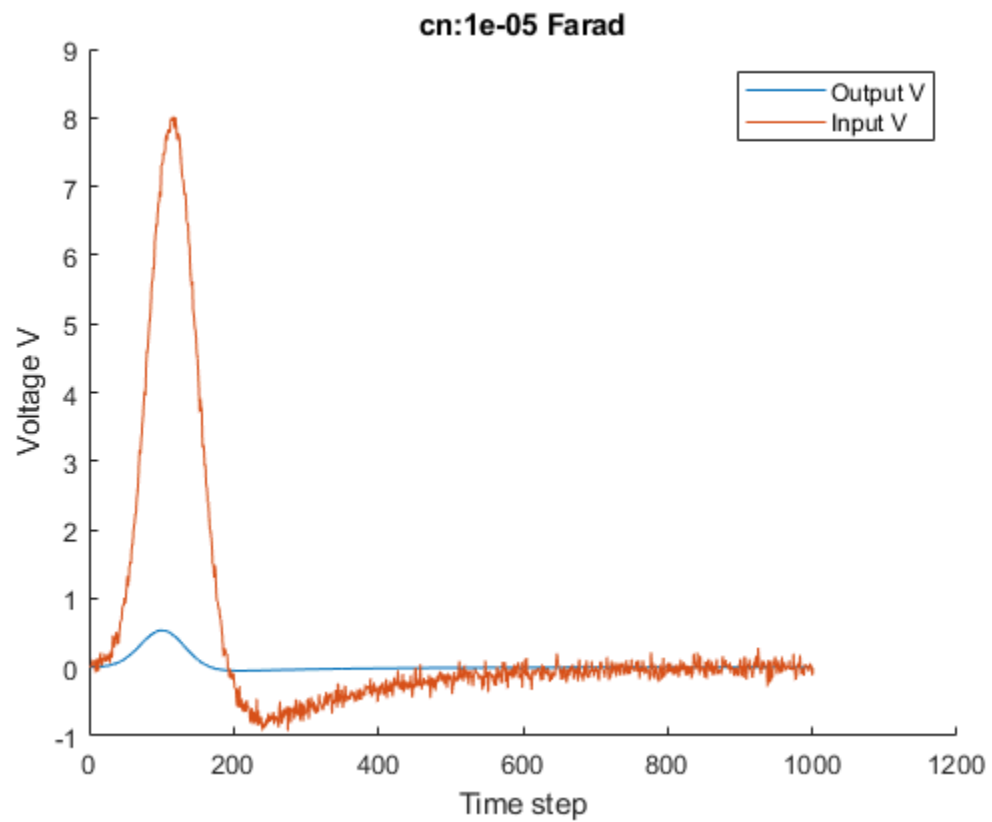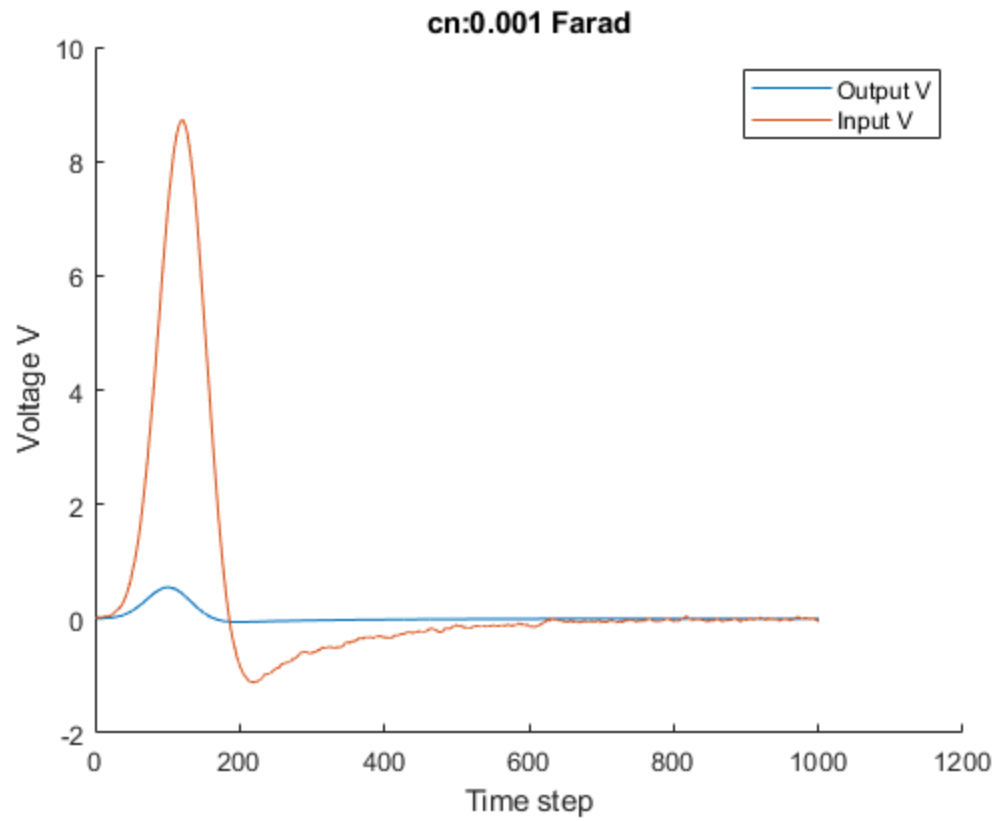

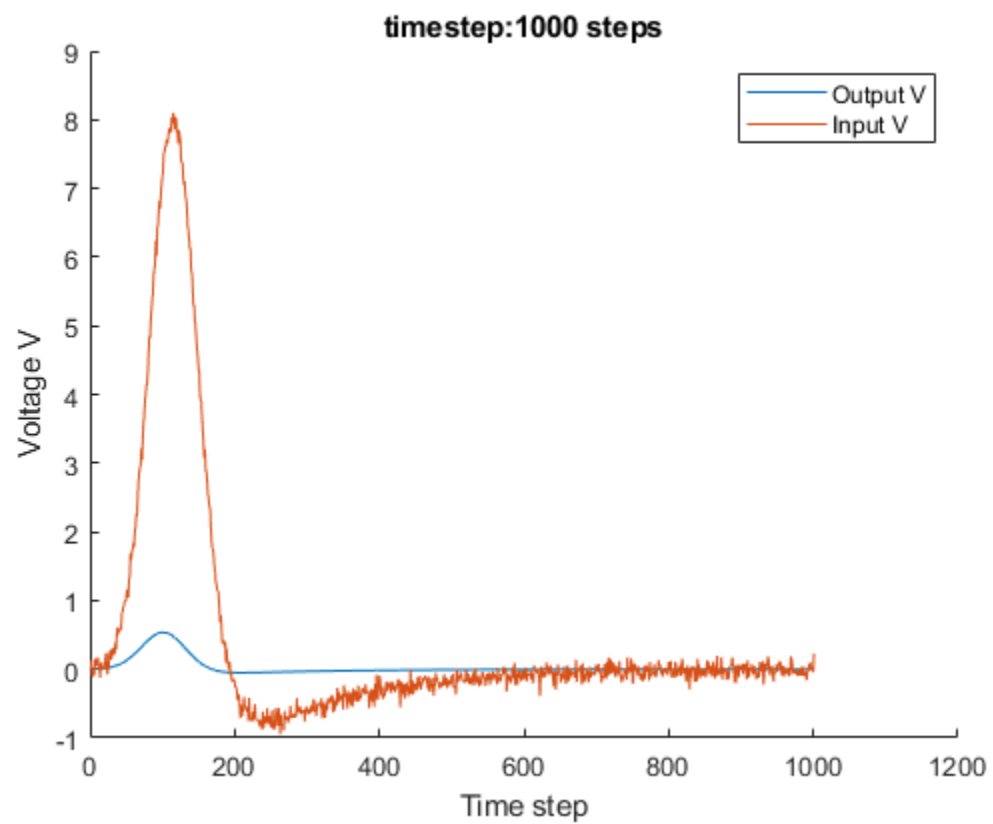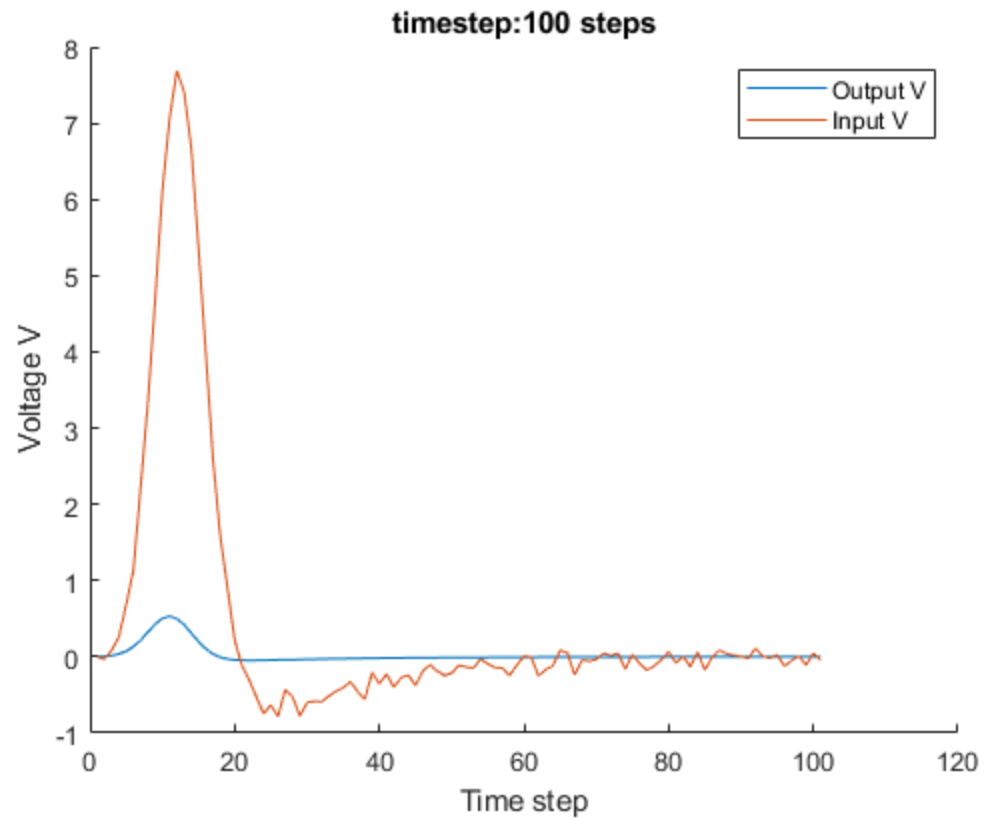

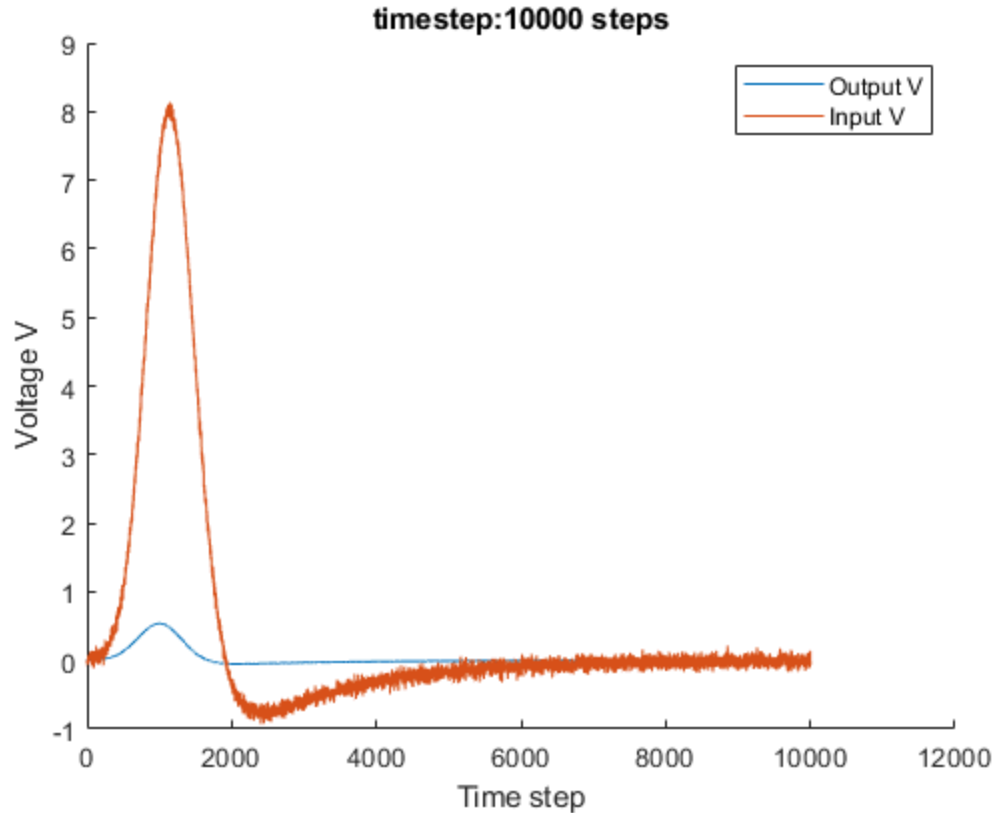

In figure 17 and 18, the noticeable addition of thermal noise can be seen. The effects of varying the C_n capacitor were noticeable as increasing the value allowed for larger noise variations on the signal. This makes sense because the capacitor should limit noise bandwidth similarly to how an RC circuit dampens abrupt changes in an electrical system. A larger capacitor resulted in larger noise variations and smaller capacitor values reduced the noise bandwidth.

As the the granularity of the time steps was increased I saw better resolution of the signal. The noise injected on the signal was easier to see at a smaller time step. Thus for maximum analysis resolution the time step should be small.

Part 4 Non Linearity

Since we now have a non linear circuit response we need to modify our analysis methods. As seen in lecture of week 10 Circuits and MNA we briefly covered some non linear analysis.

Now that we have non linear components we will need to construct the equation from slide 20, week 10.

$$\hat{C} \frac{d\hat{V}}{dt} + \hat{G}\hat{V} + \hat{B}(\hat{V}) = \hat{F}(t)$$

The B term will contain the non linear components. Since our equation is non linear we have to find the solution iteratively. We can do this by re-formulating it as a "root" finding problem and use the Newton Raphson Method.

Netwon Raphson Method :

$$x_{n+1} = x_n - \frac{f(x_n)}{\frac{df}{dx}(x_n)}$$

We also need to form the Jacobian which contains partial derivatives of the each equation in B.

Finally we can constuct the equation from slide 23, week 10.

$$\left(\frac{C}{\Delta t}\right)V_n - \frac{C}{\Delta t}V_{n-1} - B(V) - F(t) = 0$$

With the above equation, we will expand around V_n , form the Jacobian, apply the newton raphson method and and iterate for each time step to find the voltage.

Published with MATLAB® R2018b